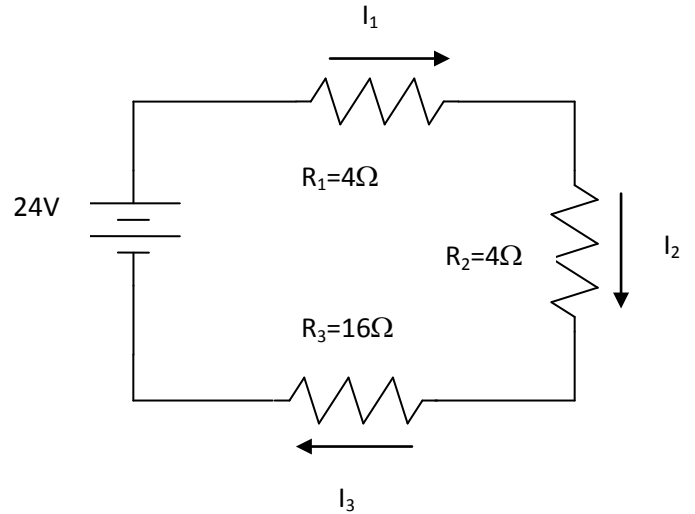


# Circuit Worksheet I

For each of the following circuits, find the total voltage, current, and resistance, as well as the voltage across each resistor, and the current through each resistor.


1.

	V	I	R	P
1				
2				
3				
totals				




2.

	V	I	R	P
1				
2				
3				
totals				

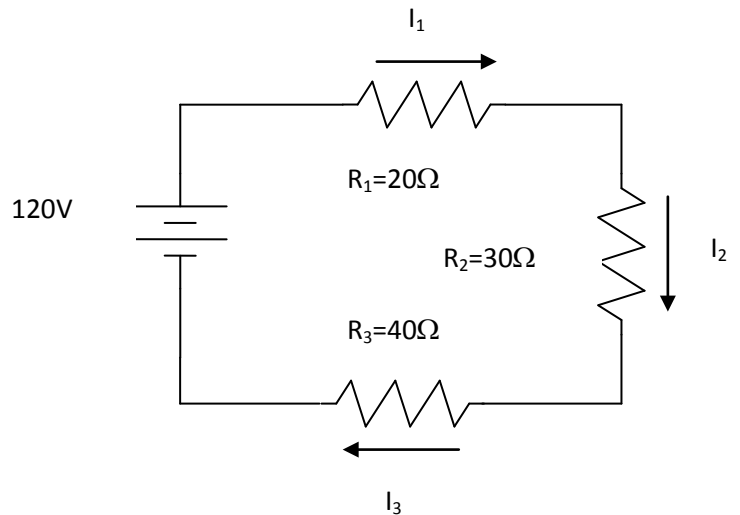


3.

	V	I	R	P
1				
2				
3				
totals				

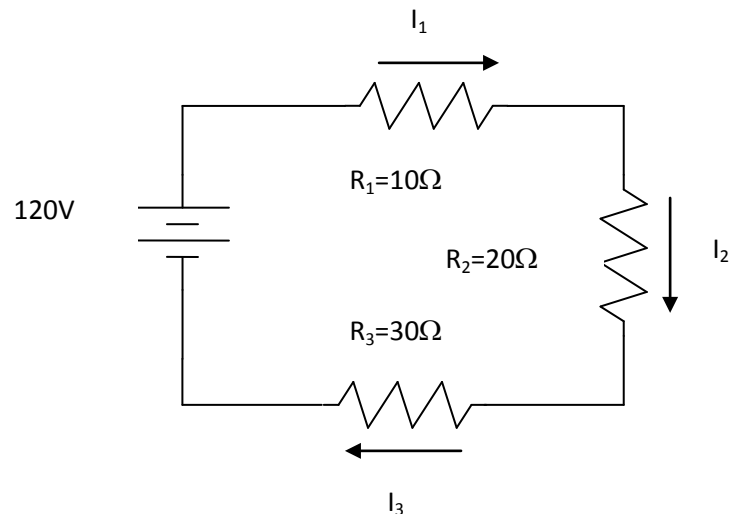


4.

	V	I	R	P
1				
2				
3				
totals				

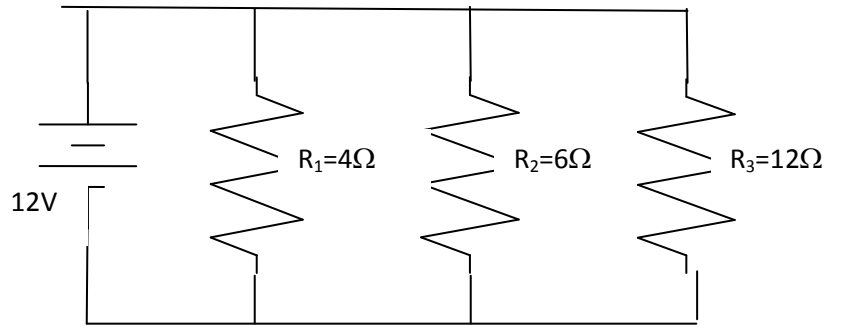

5.

	V	I	R	P
1				
2				
3				
totals				

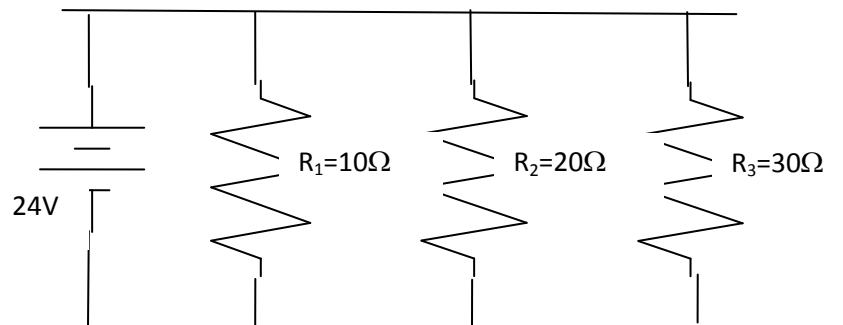

6.

	V	I	R	P
1				
2				
3				
totals				

